

# Hartley Oscillator

Harsh kabra \*

1. Find the frequency of oscillation for given hartley circuit and also find condition on  $g_m$ .  
Below is the figure, Fig 1

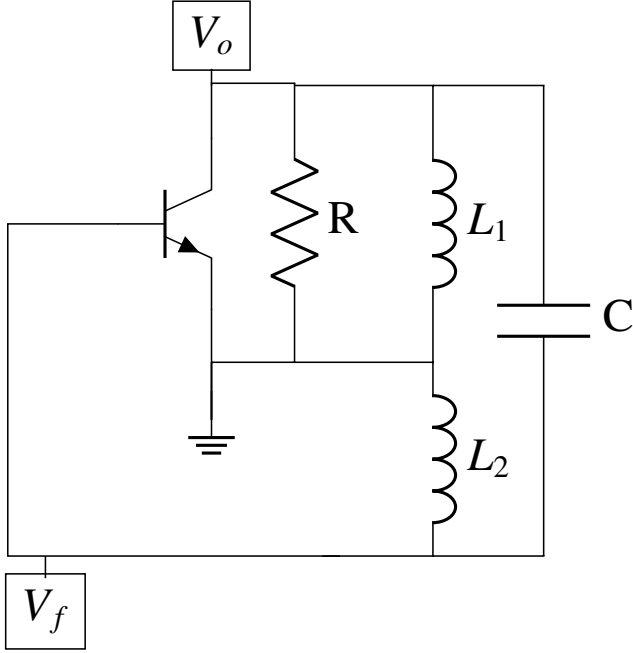


Fig. 1: Hartley oscillator

**Solution:** We will first draw an equivalent circuit for the above circuit.

To draw an equivalent block diagram we will draw small signal model for transistor Fig.1

And, its block diagram is as follows:

Here  $G(s)$  is the amplification gain, and  $H(s)$  is the feedback gain.

$G(s)$  small signal circuit is given as follows:

As,  $V_f = V_i$

and  $G(s)$  is given by,  $\frac{V_o}{V_i}$

Here,

$$i_1 = \frac{V_i}{sL_2} \quad (1.1)$$

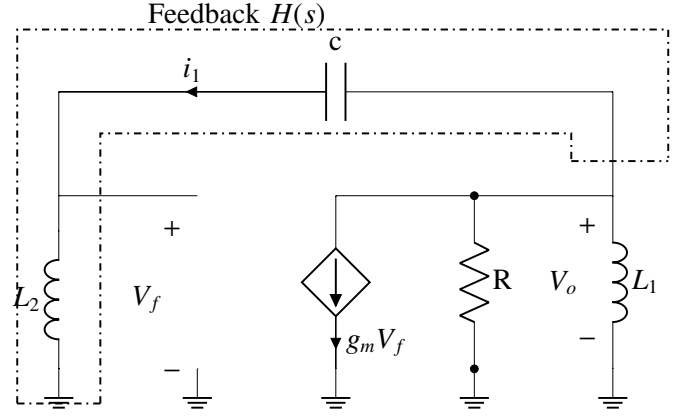


Fig. 1: Small signal model

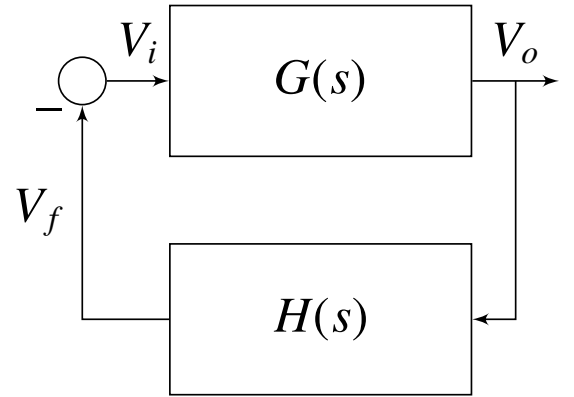


Fig. 1: Block diagram

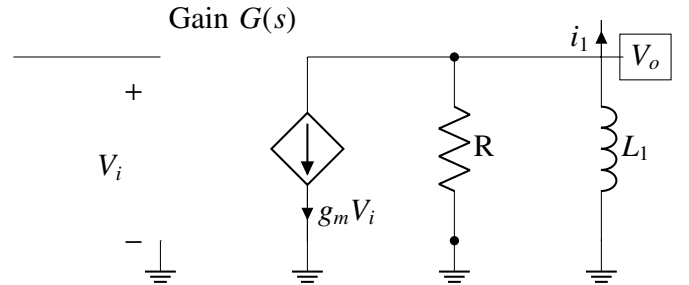


Fig. 1: Small signal  $G(s)$

$$V_o = I(sL_1 \parallel R) \quad (1.2)$$

$$I = i_1 + g_m V_i \quad (1.3)$$

Solving these equations we get,

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

$$\frac{V_o}{V_i} = G(s) = \left( g_m + \frac{1}{sL_2} \right) \left( \frac{RsL_1}{R + sL_1} \right) \quad (1.4)$$

Now, solving for H(s)

From the small signal model feedback, we know that H(s) is output/input,

Where,

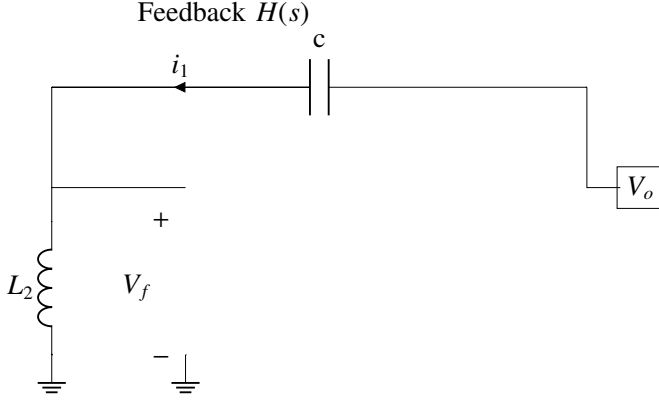


Fig. 1: Small signal H(s)

Output is  $V_f$

Input is  $V_o$

$$H(s) = \frac{V_f}{V_o} \quad (1.5)$$

$$V_o = V_f + i_1 \times \frac{1}{sC} \quad (1.6)$$

$$i_1 = \frac{V_f}{sL_2} \quad (1.7)$$

$$(1.8)$$

Solving,

$$H(s) = \left( \frac{s^2 CL_2}{s^2 CL_2 + 1} \right) \quad (1.9)$$

Characteristic equation is given by:

$$1 + G(s)H(s) = 0 \quad (1.10)$$

Substituting the values and simplifying, we get

$$s^3(g_m CL_1 L_2 + CL_1 L_2) + s^2(RCL_1 + RCL_2) + sL_1 + R = 0 \quad (1.11)$$

Now, for it to oscillate, roots of the equation should lie on imaginary axis, therefore  $j\omega$

should be a solution

Substituting that, we get

$$(R - \omega^2(RC(L_1 + L_2))) + j(\omega L_1 - \omega^3(g_m R + 1)CL_1 L_2) = 0 \quad (1.12)$$

**Equating Real part to 0**

$$\omega^2(RC(L_1 + L_2)) = R \quad (1.13)$$

$$\omega = \frac{1}{\sqrt{C(L_1 + L_2)}} \quad (1.14)$$

**Equating Imaginary part to 0**

$$g_m R + 1 = \frac{C(L_1 + L_2)}{CL_2} \quad (1.15)$$

$$g_m R = \frac{L_1}{L_2} \quad (1.16)$$

Therefore to have stable oscillations, we need  $g_m R \geq \frac{L_1}{L_2}$

### Simulation

For simulation more elaborate circuit of Hartley oscillator was used, i.e. more passive components like capacitors and resistors, so as the the oscillations don't die out quickly, and a voltage source so as the oscillations start.

Below is the circuit which was used 1

**Table for parameter values taken Verifying**

Parameter	Value
$R_1$	1.2kΩ
$R_2$	50.5kΩ
$R_3$	10.5kΩ
$R_3$	298Ω
$C_1$	22μF
$C_2$	22μF
$C$	1.1μF
$L_1$	1mH
$L_2$	1mH

TABLE 1

**the output:**

Plot generated from transfer function, taking impulse response

?? Taking an equivalent R

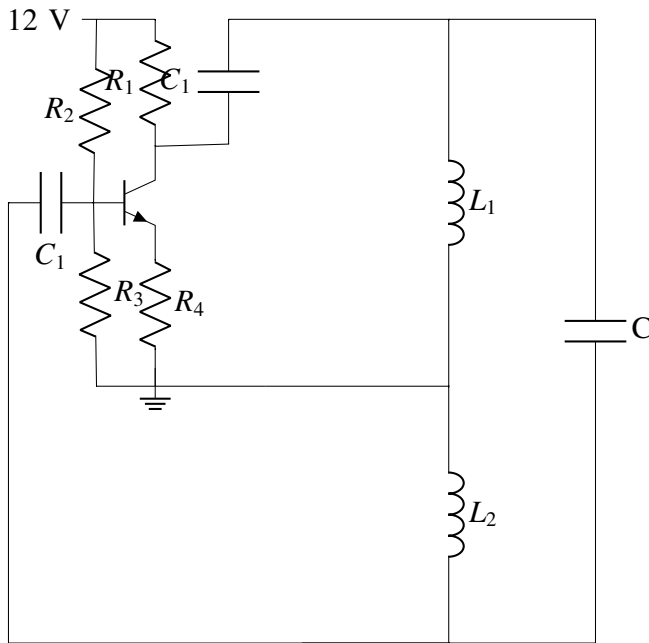


Fig. 1: Simulation circuit

$$R = L_1 \text{ and } g_m R = \frac{L_1}{L_2}$$

**Code for generating impulse response**

```
codes/ee18btech11019_1.py
```

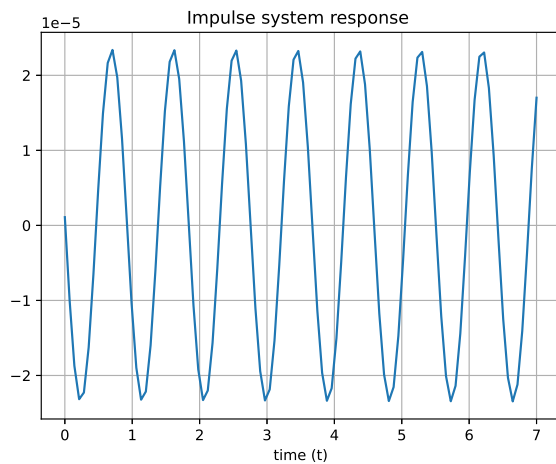


Fig. 1: Output when taken from transfer function

**Actual simulation results,**

Running ngspice netlist file, we produce dat file. From that data we get plot and frequency from python script found in

```
spice/ee18btech11019_2.py
```

Plot:

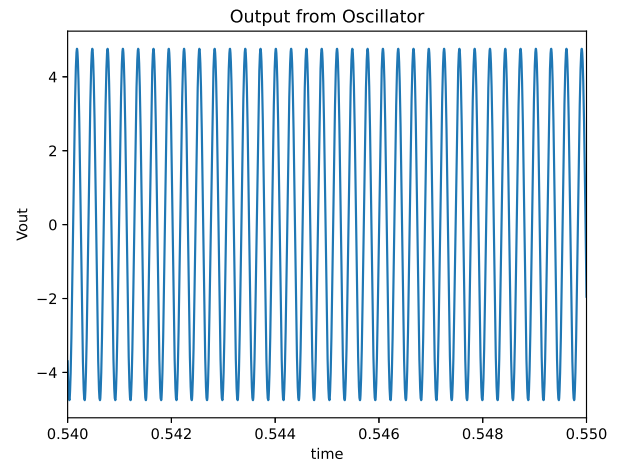


Fig. 1: Simulation result

Frequency obtained is **3384 Hz**

**Actual expected frequency is:**

$$= \frac{\omega}{2\pi} = \frac{1}{2\pi \sqrt{C(L_1 + L_2)}} \quad (1.17)$$

$$= 3394 \text{ Hz} \quad (1.18)$$